

Lab 9-10 – Nano Processor Design

Group 59

❖ Team members:

210613U-S.M.C.R. Siriwardhana:

- Register Bank
- 8-way 4-bit Mux
- Instruction decoder
- Program counter

210194H-S.L. Gunasekara

- 2-way 4-bit Mux
- 2-way 3-bit Mux
- 3-bit Adder
- 4-bit Add/Sub unit

❖ Lab Task:

design a 4-bit processor as given in the Lab capable of executing 4 instructions.

❖ Assembly Program

"100010001010", -- Movi R1,10

"100100000001", -- Movi R2,1

"010100000000", -- Neg R2

"100000000000", -- Movi R0,0

"000010100000", -- Add R1,R2

"110010000111", -- Jzr R1,7

"110000000011" -- Jzr R0,3

➤ 2-way 3-bit Mux – Design code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity mux_2_to_3 is
    Port ( r0 : in STD_LOGIC_VECTOR (2 downto 0);
          r1 : in STD_LOGIC_VECTOR (2 downto 0);
          o : out STD_LOGIC_VECTOR (2 downto 0);
          s : in STD_LOGIC);
end mux_2_to_3;

architecture Behavioral of mux_2_to_3 is

begin
    o <= r0 when s='0' else r1;
end Behavioral;
```

- Test bench code:

```
entity TB_mux_2_to_3 is
-- Port ( );
end TB_mux_2_to_3;

architecture Behavioral of TB_mux_2_to_3 is
component mux_2_to_3
    Port ( r0 : in STD_LOGIC_VECTOR (2 downto 0);
          r1 : in STD_LOGIC_VECTOR (2 downto 0);
          o : out STD_LOGIC_VECTOR (2 downto 0);
          s : in STD_LOGIC);
end component;

signal r0: STD_LOGIC_VECTOR (2 downto 0);
signal r1: STD_LOGIC_VECTOR (2 downto 0);
signal o: STD_LOGIC_VECTOR (2 downto 0);
signal s: STD_LOGIC;

begin

uut:mux_2_to_3
    port map(
        r0=>r0,
        r1=>r1,
        o=>o,
        s=>s);


PROCESS
BEGIN

    r0<="110";
    r1<="101";
```

```
s<='0';  
  
wait for 20ns;  
  
s<='1';  
  
wait;  
  
END PROCESS;
```

end Behavioral;

simulation:

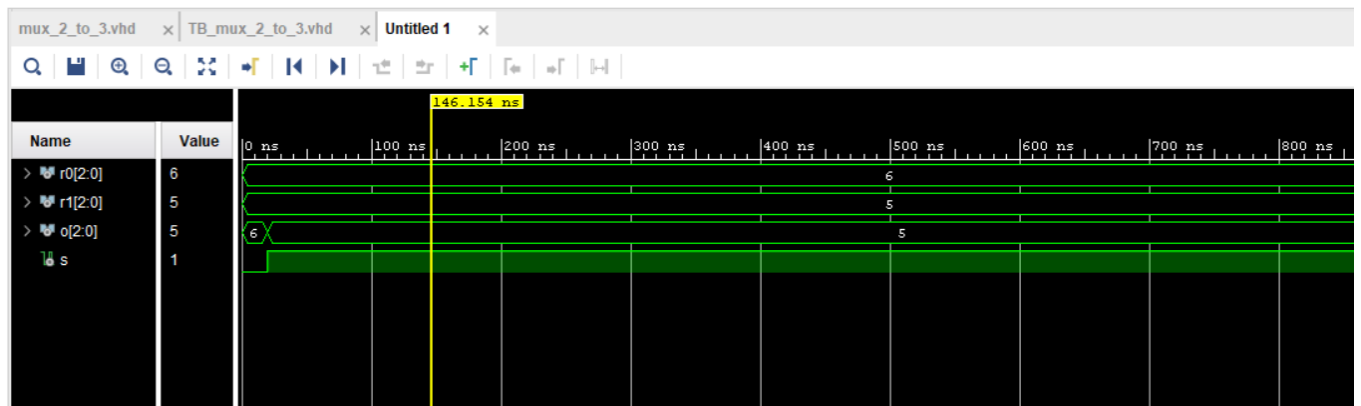

➤ 2-way 4-bit Mux- Design code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity mux_2_to_4 is
Port ( r0 : in STD_LOGIC_VECTOR (3 downto 0);
      r1 : in STD_LOGIC_VECTOR (3 downto 0);
      o : out STD_LOGIC_VECTOR (3 downto 0);
      s : in STD_LOGIC);
end mux_2_to_4;

architecture Behavioral of mux_2_to_4 is

begin
o <= r0 when s='0' else r1;
end Behavioral;
```

- Test bench code

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;


-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;


-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;


entity TB_mux_2_to_4 is
-- Port ( );
end TB_mux_2_to_4;


architecture Behavioral of TB_mux_2_to_4 is
component mux_2_to_4
    Port ( r0 : in STD_LOGIC_VECTOR (3 downto 0);
          r1 : in STD_LOGIC_VECTOR (3 downto 0);
          o : out STD_LOGIC_VECTOR (3 downto 0);
          s : in STD_LOGIC);
end component;

    signal r0: STD_LOGIC_VECTOR (3 downto 0);
    signal r1: STD_LOGIC_VECTOR (3 downto 0);
    signal o: STD_LOGIC_VECTOR (3 downto 0);
    signal s: STD_LOGIC;
```

```
begin
```

```
  uut:mux_2_to_4
```

```
    port map(
```

```
      r0=>r0,
```

```
      r1=>r1,
```

```
      o=>o,
```

```
      s=>s);
```

```
PROCESS
```

```
BEGIN
```

```
  r0<="1100";
```

```
  r1<="1111";
```

```
  s<='0';
```

```
  wait for 20ns;
```

```
  s<='1';
```

```
  wait;
```

```
END PROCESS;
```

```
end Behavioral;
```

simulation:



➤ 8-way 4-bit Mux – Design code

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity Mux_8_Way_Double is
    Port ( r0 : in STD_LOGIC_VECTOR (3 downto 0);
          r1 : in STD_LOGIC_VECTOR (3 downto 0);
          r2 : in STD_LOGIC_VECTOR (3 downto 0);
          r3 : in STD_LOGIC_VECTOR (3 downto 0);
          r4 : in STD_LOGIC_VECTOR (3 downto 0);
          r5 : in STD_LOGIC_VECTOR (3 downto 0);
          r6 : in STD_LOGIC_VECTOR (3 downto 0);
          r7 : in STD_LOGIC_VECTOR (3 downto 0);
          oa : out STD_LOGIC_VECTOR (3 downto 0);
          ob : out STD_LOGIC_VECTOR (3 downto 0);
          sa : in STD_LOGIC_VECTOR (2 downto 0);
          sb : in STD_LOGIC_VECTOR (2 downto 0));
end Mux_8_Way_Double;
```

architecture Behavioral of Mux_8_Way_Double is

begin

process (sa, r0, r1, r2, r3, r4, r5, r6, r7)

begin

if sa="000" then

oa <= r0;

elsif sa="001" then

oa <= r1;

elsif sa="010" then

oa <= r2 ;

elsif sa="011" then

oa <= r3;

elsif sa="100" then

oa <= r4;

elsif sa="101" then

oa <= r5;

elsif sa="110" then

oa <= r6;

else

oa <= r7;

end if;

end process;

process (sb, r0, r1, r2, r3, r4, r5, r6, r7)

begin

if sb="000" then

ob <= r0;

```
elseif sb="001" then
```

```
    ob <= r1;
```

```
elseif sb="010" then
```

```
    ob <= r2 ;
```

```
elseif sb="011" then
```

```
    ob <= r3;
```

```
elseif sb="100" then
```

```
    ob <= r4;
```

```
elseif sb="101" then
```

```
    ob <= r5;
```

```
elseif sb="110" then
```

```
    ob <= r6;
```

```
else
```

```
    ob <= r7;
```

```
end if;
```

```
end process;
```

```
end Behavioral;
```

- Test bench code:

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;


-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;


-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;


entity TB_Mux_8_Way_Double is
-- Port ( );
end TB_Mux_8_Way_Double;


architecture Behavioral of TB_Mux_8_Way_Double is

component Mux_8_Way_Double is
    Port ( r0 : in STD_LOGIC_VECTOR (3 downto 0);
          r1 : in STD_LOGIC_VECTOR (3 downto 0);
          r2 : in STD_LOGIC_VECTOR (3 downto 0);
          r3 : in STD_LOGIC_VECTOR (3 downto 0);
          r4 : in STD_LOGIC_VECTOR (3 downto 0);
          r5 : in STD_LOGIC_VECTOR (3 downto 0);
          r6 : in STD_LOGIC_VECTOR (3 downto 0);
          r7 : in STD_LOGIC_VECTOR (3 downto 0);
```

```

        oa : out STD_LOGIC_VECTOR (3 downto 0);
        ob : out STD_LOGIC_VECTOR (3 downto 0);
        sa : in STD_LOGIC_VECTOR (2 downto 0);
        sb : in STD_LOGIC_VECTOR (2 downto 0));
end component;

signal r0, r1, r2, r3, r4, r5, r6, r7, oa, ob : STD_LOGIC_VECTOR (3 downto 0);
signal sa, sb : STD_LOGIC_VECTOR (2 downto 0);

begin

mux_8_way_double_1: Mux_8_Way_Double port map(
    r0=>r0,
    r1=>r1,
    r2=>r2,
    r3=>r3,
    r4=>r4,
    r5=>r5,
    r6=>r6,
    r7=>r7,
    oa=>oa,
    ob=>ob,
    sa=>sa,
    sb=>sb);

PROCESS
BEGIN
    r0<="1100";
    r1<="1111";

```

```
r2<="1011";
```

```
r3<="0111";
```

```
r4<="1101";
```

```
r5<="1001";
```

```
r6<="0100";
```

```
r7<="0111";
```

```
sa<="001";
```

```
sb<="010";
```

```
wait for 20ns;
```

```
sa<="010";
```

```
sb<="100";
```

```
wait for 20ns;
```

```
sa<="100";
```


```
sb<="000";
```

```
wait;
```

```
END PROCESS;
```

```
end Behavioral;
```

simulation:

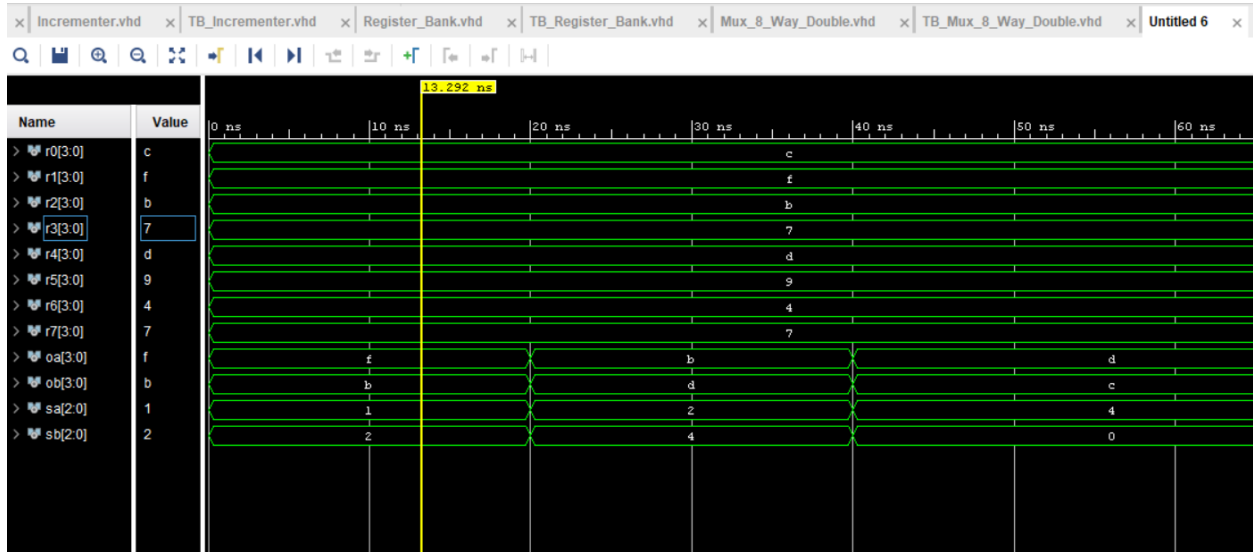



➤ Arithmetic unit – Design code

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.

entity Arithmetic_Unit is
    Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
          B : in STD_LOGIC_VECTOR (3 downto 0);
          Add_Sub_Sel : in STD_LOGIC;
          S : out STD_LOGIC_VECTOR (3 downto 0);
          C_out : out STD_LOGIC;
          Zero : out STD_LOGIC);
    -- attribute use_dsp : string;
    -- attribute use_dsp of Arithmetic_Unit : entity is "yes";
end Arithmetic_Unit;

architecture Behavioral of Arithmetic_Unit is

    component AddSubUnit Port (
        a:in std_logic_vector (3 downto 0);
        b:in std_logic_vector (3 downto 0);
```



```
s:out std_logic_vector (3 downto 0);  
add : in STD_LOGIC;  
c_out : out STD_LOGIC);  
end component;  
  
signal O : STD_LOGIC_VECTOR (3 downto 0);  
  
begin  
  
add_sub_unit_0 : AddSubUnit  
port map (  
A => B,  
B => A,  
ADD => Add_Sub_Sel,  
C_OUT => C_out,  
S => O);  
  
S <= O;  
Zero <= NOR(O);  
  
end Behavioral;
```

- Test bench code

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity TB_Arithmetic_Unit is
-- Port ( );
end TB_Arithmetic_Unit;

architecture Behavioral of TB_Arithmetic_Unit is

component Arithmetic_Unit port
( a:in std_logic_vector (3 downto 0);
  b:in std_logic_vector (3 downto 0);
  s:out std_logic_vector (3 downto 0);
  Add_Sub_Sel : in STD_LOGIC;
  zero : out STD_LOGIC;
  C_out : out STD_LOGIC);
end component;
```

```
signal a,b,s:std_logic_vector (3 downto 0);  
signal overflow,Add_Sub_Sel,zero:std_logic;
```

```
begin
```

```
uut : Arithmetic_Unit port map(
```

```
a=>a,
```

```
b=>b,
```

```
s=>s,
```

```
c_out=>overflow,
```

```
zero=>zero,
```

```
Add_Sub_Sel=>Add_Sub_Sel);
```

```
process
```

```
begin
```

```
Add_Sub_Sel<='0';
```

```
a<="1111";
```

```
b<="0101";
```

```
wait for 20ns;
```

```
Add_Sub_Sel<='1';
```

```
a<="1111";
```

```
b<="0011"; --randomly selected
```

```
wait for 20ns;
```

```
Add_Sub_Sel<='0';
```

```
a<="0000";
```

```
b<="0000";
```

```
wait;
```

```
end process;
```

```
end Behavioral;
```

Simulation:



➤ Incrementor -Design code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity Incrementer is
    Port ( A:in std_logic_vector (2 downto 0);
          S:out std_logic_vector (2 downto 0));
    --    attribute use_dsp : string;
    --    attribute use_dsp of Incrementer : entity is "yes";

end Incrementer;

architecture Behavioral of Incrementer is

begin
    S <= A + 1;
end Behavioral;
```

- Test bench code:

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;


-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;


-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;


entity TB_Incrementer is
-- Port ( );
end TB_Incrementer;


architecture Behavioral of TB_Incrementer is


component Incrementer
    Port ( A : in STD_LOGIC_VECTOR (2 downto 0);
          S : out STD_LOGIC_VECTOR (2 downto 0));
end component;

 

signal A, S : STD_LOGIC_VECTOR (2 downto 0);


begin


UUT : Incrementer
```

```
port map (  
    A => A,  
    S => S);  
  
process begin  
    A <= "000";  
    wait for 10 ns;  
    A <= "001";  
    wait for 10 ns;  
    A <= "010";  
    wait for 10 ns;  
    A <= "011";  
    wait for 10 ns;  
    A <= "100";  
    wait for 10 ns;  
    A <= "101";  
    wait for 10 ns;  
    A <= "110";  
    wait for 10 ns;  
    A <= "111";  
    wait for 10 ns;  
    wait;  
  
end process;  
  
end Behavioral;
```

simulation:



➤ Register bank – Design code:

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;


-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;


-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;


entity Register_Bank is
    Port ( data : in STD_LOGIC_VECTOR (3 downto 0);
          clk : in STD_LOGIC;
          en : in STD_LOGIC_VECTOR (2 downto 0);
          r0 : out STD_LOGIC_VECTOR (3 downto 0) := "0000";
          r1 : out STD_LOGIC_VECTOR (3 downto 0);
          r2 : out STD_LOGIC_VECTOR (3 downto 0);
          r3 : out STD_LOGIC_VECTOR (3 downto 0);
          r4 : out STD_LOGIC_VECTOR (3 downto 0);
          r5 : out STD_LOGIC_VECTOR (3 downto 0);
          r6 : out STD_LOGIC_VECTOR (3 downto 0);
          r7 : out STD_LOGIC_VECTOR (3 downto 0));
end Register_Bank;


architecture Behavioral of Register_Bank is
```

```
component reg port(  
    D : in STD_LOGIC_VECTOR (3 downto 0);  
    en : in STD_LOGIC;  
    clk : in STD_LOGIC;  
    Q : out STD_LOGIC_VECTOR (3 downto 0));  
end component;
```

```
component decoder_3_to_8  
Port ( I : in STD_LOGIC_VECTOR (2 downto 0);  
    Y : out STD_LOGIC_VECTOR (7 downto 0));  
end component;
```

```
signal d_en:std_logic_vector (7 downto 0);
```

```
begin
```

```
dec:decoder_3_to_8 port map(  
    i=>en,  
    y=>d_en);
```

```
reg1:reg port map(  
    d=>data,  
    en=>d_en(1),  
    clk=>clk,  
    q=>r1);
```

```
reg2:reg port map(  
    d=>data,  
    en=>d_en(2),  
    clk=>clk,
```

```
    q=>r2);
reg3:reg port map(
    d=>data,
    en=>d_en(3),
    clk=>clk,
    q=>r3);
reg4:reg port map(
    d=>data,
    en=>d_en(4),
    clk=>clk,
    q=>r4);
reg5:reg port map(
    d=>data,
    en=>d_en(5),
    clk=>clk,
    q=>r5);
reg6:reg port map(
    d=>data,
    en=>d_en(6),
    clk=>clk,
    q=>r6);
reg7:reg port map(
    d=>data,
    en=>d_en(7),
    clk=>clk,
    q=>r7);

end Behavioral;
```

- Test bench code:

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;


-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;


-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;


entity TB_Register_Bank is
-- Port ( );
end TB_Register_Bank;


architecture Behavioral of TB_Register_Bank is


component Register_bank
port (data : in STD_LOGIC_VECTOR (3 downto 0);
      clk : in STD_LOGIC;
      en : in STD_LOGIC_VECTOR (2 downto 0);
      r0 : out STD_LOGIC_VECTOR (3 downto 0);
      r1 : out STD_LOGIC_VECTOR (3 downto 0);
      r2 : out STD_LOGIC_VECTOR (3 downto 0);
      r3 : out STD_LOGIC_VECTOR (3 downto 0);
      r4 : out STD_LOGIC_VECTOR (3 downto 0);
      r5 : out STD_LOGIC_VECTOR (3 downto 0);
```

```

        r6 : out STD_LOGIC_VECTOR (3 downto 0);
        r7 : out STD_LOGIC_VECTOR (3 downto 0));
end component;

signal data : STD_LOGIC_VECTOR (3 downto 0);
signal r0, r1, r2, r3, r4, r5, r6, r7 : STD_LOGIC_VECTOR (3 downto 0) := "0000";
signal clk : STD_LOGIC := '0';
signal en : STD_LOGIC_VECTOR (2 downto 0);

begin

    uut: Register_bank
        Port map (
            data=>data,
            clk=>clk,
            en=>en,
            r0=>r0,
            r1=>r1,
            r2=>r2,
            r3=>r3,
            r4=>r4,
            r5=>r5,
            r6=>r6,
            r7=>r7);

    process
    begin
        wait for 5ns;

        clk <= NOT clk;
    end process;

```

```
process
begin
    data <= "1011";

    en <= "111";
    wait for 20ns;


    en <= "011";
    wait for 20ns;

    en <= "101";
    wait for 20ns;

    en <= "110";
    wait;

end process;
end Behavioral;
```

Simulation:

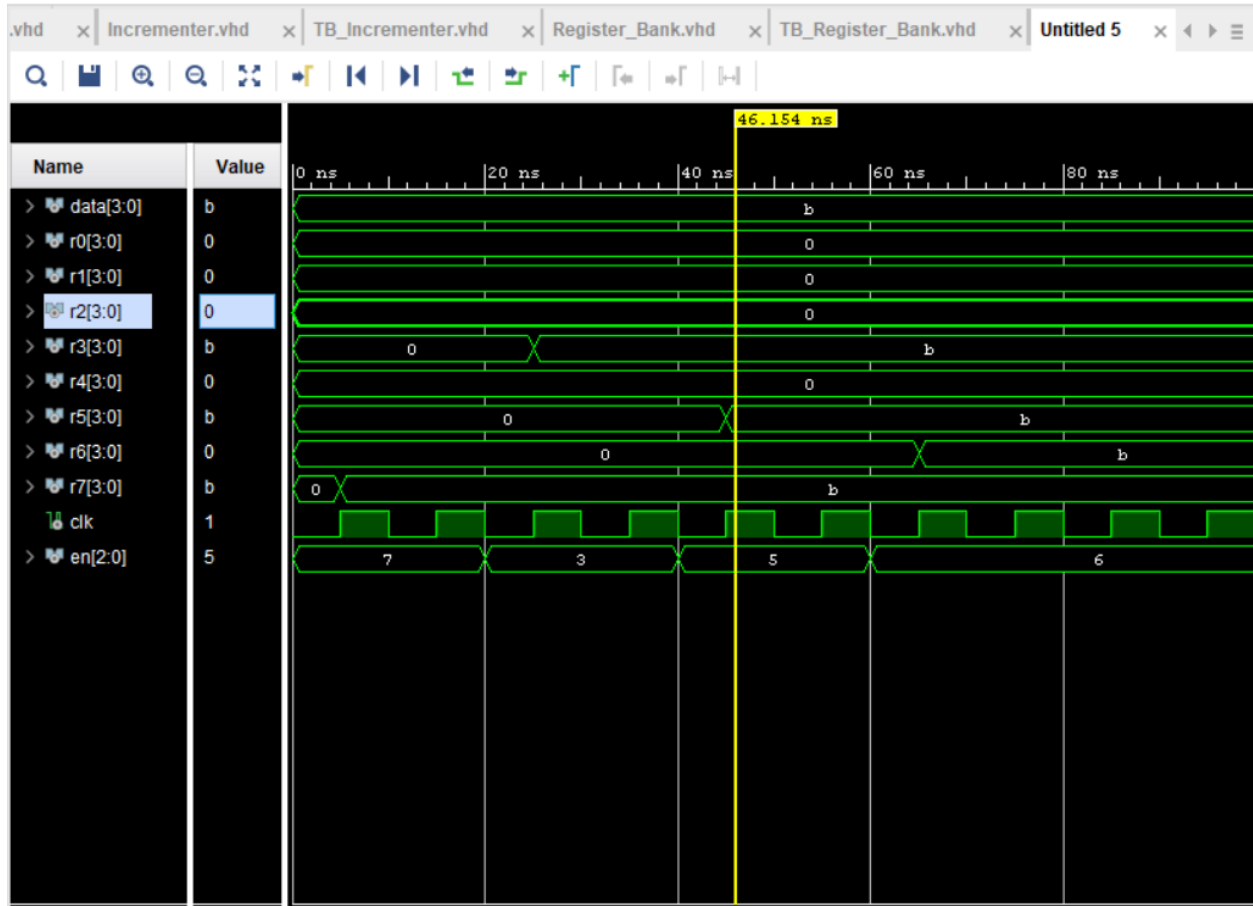

➤ Instruction decoder – Design code

library IEEE;

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Uncomment the following library declaration if using
```

```
-- arithmetic functions with Signed or Unsigned values
```

```
--use IEEE.NUMERIC_STD.ALL;
```

```
-- Uncomment the following library declaration if instantiating
```

```
-- any Xilinx leaf cells in this code.
```

```
--library UNISIM;
```

```
--use UNISIM.VComponents.all;
```

```
entity Instruction_Decoder is
```

```
    Port (
```

```
        ins : in STD_LOGIC_VECTOR (11 downto 0);
```

```
        reg_en : out STD_LOGIC_VECTOR (2 downto 0) := "000";
```

```
        load_sel : out STD_LOGIC := '0';
```

```
        value : out STD_LOGIC_vector (3 downto 0) := "0000";
```

```
        mux_1 : out STD_LOGIC_VECTOR (2 downto 0) := "000";
```

```
        mux_2 : out STD_LOGIC_VECTOR (2 downto 0) := "000";
```

```
        aors : out STD_LOGIC := '0';
```

```
        jmp_flg : out STD_LOGIC := '0';
```

```
        jmp_add : out std_logic_vector (2 downto 0) := "000";
```

```
        check : in STD_LOGIC := '0');
```

```
--        attribute use_dsp : string;
```

```
--        attribute use_dsp of Instruction_Decoder : entity is "yes";
```

```
end Instruction_Decoder;
```

```
architecture Behavioral of Instruction_Decoder is
```



```
signal first_2_bits : std_logic_vector (1 downto 0);
```

```
begin
```

```
process (ins, check, first_2_bits)
```

```
begin
```

```
reg_en <= ins(9 downto 7);
```

```
jmp_add <= ins(2 downto 0);
```

```
first_2_bits <= ins(11 downto 10);
```

```
mux_1 <= ins(9 downto 7);
```

```
mux_2<=ins(6 downto 4);
```

```
value<=ins(3 downto 0);
```

```
if first_2_bits = "00" then
```

```
    aors<='1';
```

```
    load_sel<='0';
```

```
    jmp_flg<='0';
```

```
elsif first_2_bits = "01" then
```

```
    aors<='0';
```

```
    load_sel<='0';
```

```
    jmp_flg<='0';
```

```
elsif first_2_bits = "10" then
```

```
    aors<='1';
```

```
    load_sel<='1';
```

```
    jmp_flg<='0';
```

```
else
```

```
    aors<='1';
```

```
    load_sel<='0';
```

```
    jmp_flg<=check;  
end if;
```

```
end process;
```

```
end Behavioral;
```

Test bench code:

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;


-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;


-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;


entity TB_Instruction_Decoder is
-- Port ( );
end TB_Instruction_Decoder;


architecture Behavioral of TB_Instruction_Decoder is


component Instruction_Decoder Port ( ins : in STD_LOGIC_VECTOR (8 downto 0);
    reg_en : out STD_LOGIC_VECTOR (2 downto 0);
    load : out STD_LOGIC;
    value : out STD_LOGIC_vector (3 downto 0);
    mux_1 : out STD_LOGIC_VECTOR (2 downto 0);
    mux_2 : out STD_LOGIC_VECTOR (2 downto 0);
    aors : out STD_LOGIC;
    jmp_flg : out STD_LOGIC;
    jmp_add:out std_logic_vector (2 downto 0);
    check:in std_logic_vector (3 downto 0));
end component;

```

```
signal load, aors, jmp_flg : STD_LOGIC;
signal reg_en, mux_1, mux_2, jmp_add : STD_LOGIC_VECTOR (2 downto 0);
signal value, check : STD_LOGIC_vector (3 downto 0);
signal ins : STD_LOGIC_VECTOR (8 downto 0);
```

```
begin
```

```
uut: Instruction_Decoder port map(
```

```
    ins=>ins,
    reg_en=>reg_en,
    load=>load,
    value=>value,
    mux_1=>mux_1,
    mux_2=>mux_2,
    aors=>aors,
    jmp_flg=>jmp_flg,
    jmp_add=>jmp_add,
    check=>check);
```

```
process begin
```

```
    check <= "0000";
    ins <= "001011110"; --ADD R5, R7
    wait for 5ns;

    ins <= "100101001"; --MOVI R2, 9
    wait for 5ns;
```

```
ins <= "010100000"; --NEG R2
```

```
wait for 5ns;
```

```
ins <= "110100100"; --JZR R2, 4
```

```
wait for 5ns;
```


```
check <= "1000";
```

```
wait;
```

```
end process;
```

```
end Behavioral;
```

simulation:

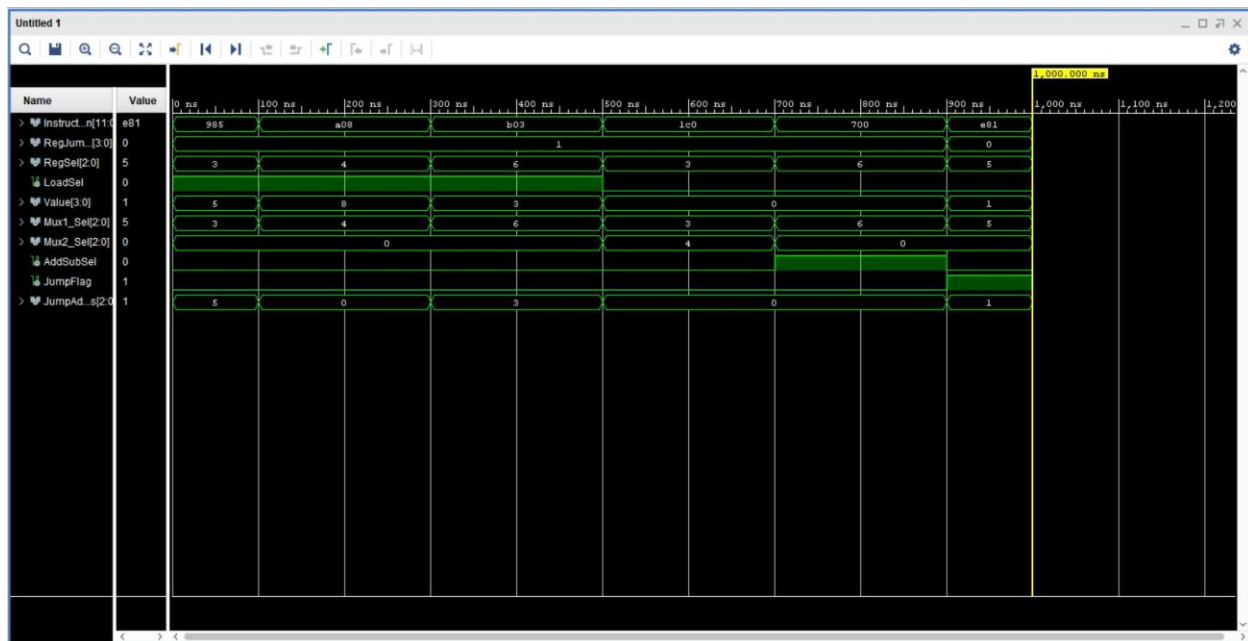

➤ Program counter – Design code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity Program_Counter is
    Port ( D : in STD_LOGIC_VECTOR (2 downto 0) := "000";
          Clk : in STD_LOGIC;
          Res : in STD_LOGIC := '0';
          Q : out std_logic_vector (2 downto 0) := "000");
    -- attribute use_dsp : string;
    -- attribute use_dsp of Program_Counter : entity is "yes";
end Program_Counter;
```

architecture Behavioral of Program_Counter is

begin

process (Clk, D) begin

if (rising_edge(Clk)) then

if Res = '1' then

Q <= "000";

else

Q <= D;

end if;

end if;

end process;

end Behavioral;

Test bench code:

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using

-- arithmetic functions with Signed or Unsigned values

--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating

-- any Xilinx leaf cells in this code.

--library UNISIM;

--use UNISIM.VComponents.all;

```

entity TB_Program_Counter is
-- Port ( );
end TB_Program_Counter;

architecture Behavioral of TB_Program_Counter is
component Program_Counter
    Port ( D : in STD_LOGIC_VECTOR (2 downto 0);
          clk : in STD_LOGIC;
          res : in STD_LOGIC ;
          Q : out std_logic_vector (2 downto 0));
end component;
signal clk : STD_LOGIC := '0';
signal res : STD_LOGIC := '0';
signal D,Q : STD_LOGIC_VECTOR (2 downto 0);

begin
UUT: Program_Counter
    port map(
        D=>D,
        clk=>clk,
        res=>res,
        Q=>Q);

process
begin
    clk<=not(clk);
    wait for 1ns;
end process;

```




```
process
begin
    wait for 80ns;
    res<=not(res);
end process;
```

```
process
begin
    D <= "000";
    wait for 10 ns;
    D <= "001";
    wait for 10 ns;
    D <= "010";
    wait for 10 ns;
    D <= "011";
    wait for 10 ns;
    D <= "100";
    wait for 10 ns;
    D <= "101";
    wait for 10 ns;
    D <= "110";
    wait for 10 ns;
    D <= "111";
    wait;
end process;
```

```
end Behavioral;
```

- Simulation:

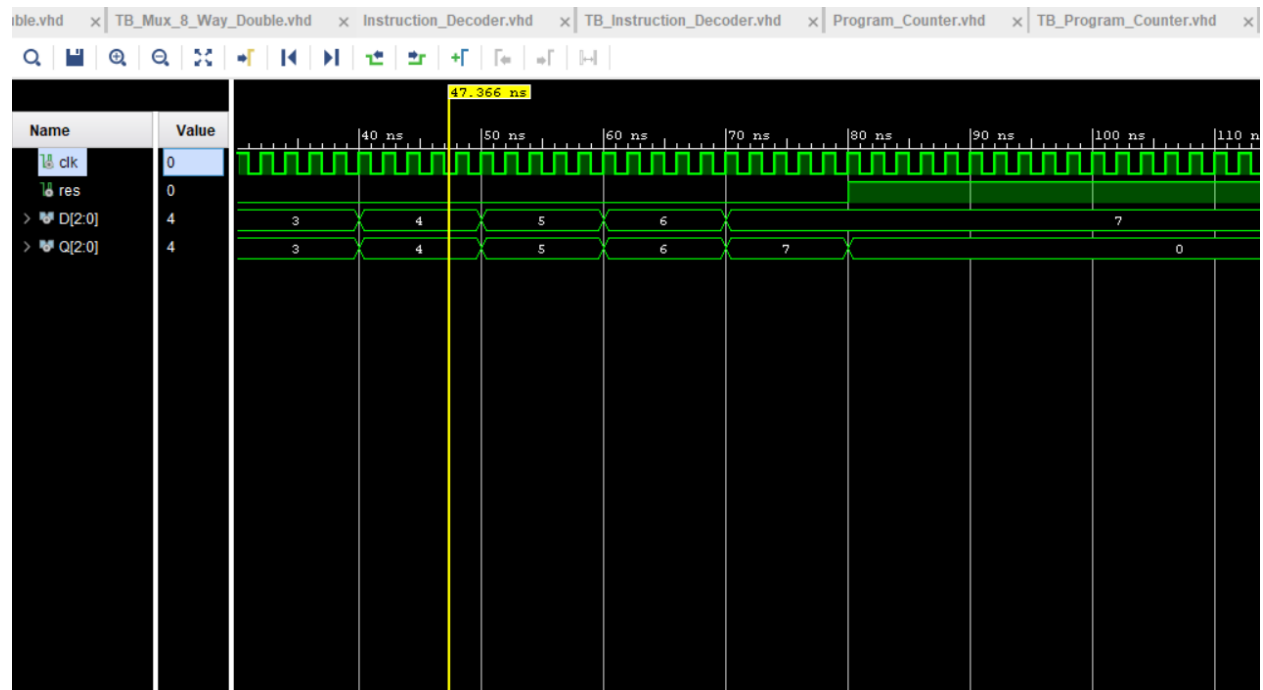

➤ ROM- Design code

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;


-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
use IEEE.NUMERIC_STD.ALL;


-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;


entity ROM is
    Port ( address : in STD_LOGIC_VECTOR (2 downto 0);
          data : out STD_LOGIC_VECTOR (11 downto 0));
end ROM;


architecture Behavioral of ROM is
    type rom_type is array (0 to 7) of std_logic_vector(11 downto 0);
    signal twelveSegment_ROM : rom_type := (
        "100010000011", --MOV R1, 3
        "100100000001", --MOV R2, 1
        "010100000000", --NEG R2
        "001110010000", --ADD R7, R1
        "000010100000", --ADD R1, R2
```

```
"110010000111", --JZR R1, 7  
"110000000011", --JZR R0, 3  
"110010000101" --JZR R1, 5  
);
```

```
begin  
data <= twelveSegment_ROM(to_integer(unsigned(address)));  
end Behavioral;
```

Test bench code:

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Uncomment the following library declaration if using  
-- arithmetic functions with Signed or Unsigned values  
--use IEEE.NUMERIC_STD.ALL;
```

```
-- Uncomment the following library declaration if instantiating  
-- any Xilinx leaf cells in this code.  
--library UNISIM;  
--use UNISIM.VComponents.all;
```

```
entity TB_ROM is
```

```
-- Port ( );
```

```
end TB_ROM;
```

```
architecture Behavioral of TB_ROM is
```

component ROM

Port (address : in STD_LOGIC_VECTOR (2 downto 0);

data : out STD_LOGIC_VECTOR (8 downto 0));

end component;

signal address: STD_LOGIC_VECTOR(2 downto 0);

signal data : STD_LOGIC_VECTOR (8 downto 0);

begin

uut: ROM

Port map (address => address,

data => data);

process

begin

address <= "111";

wait for 20ns;

address <= "011";

wait for 20ns;

address <= "101";

wait for 20ns;

address <= "000";

wait for 20ns;

```
address <= "110";
```

```
wait;
```

```
end process;
```

```
end Behavioral;
```

Simulation:

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;


-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;


-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;


entity MicroProcessor is
    Port ( reset : in STD_LOGIC := '0';
          clk : in STD_LOGIC;
          zero : out STD_LOGIC;
          overflow : out STD_LOGIC;
          led: out std_logic_vector (3 downto 0);
          S_7Seg : out STD_LOGIC_VECTOR (6 downto 0);
          Anode : out STD_LOGIC_VECTOR (3 downto 0) := "1110");
end MicroProcessor;


architecture Behavioral of MicroProcessor is


component Slow_Clock is
    Port ( Clk_in : in STD_LOGIC;
          Clk_out : out STD_LOGIC);
end component;

```

```
component Register_Bank Port ( data : in STD_LOGIC_VECTOR (3 downto 0);
```

```
    clk : in STD_LOGIC;
```

```
    en : in STD_LOGIC_VECTOR (2 downto 0);
```

```
    r0 : out STD_LOGIC_VECTOR (3 downto 0);
```

```
    r1 : out STD_LOGIC_VECTOR (3 downto 0);
```

```
    r2 : out STD_LOGIC_VECTOR (3 downto 0);
```

```
    r3 : out STD_LOGIC_VECTOR (3 downto 0);
```

```
    r4 : out STD_LOGIC_VECTOR (3 downto 0);
```

```
    r5 : out STD_LOGIC_VECTOR (3 downto 0);
```

```
    r6 : out STD_LOGIC_VECTOR (3 downto 0);
```

```
    r7 : out STD_LOGIC_VECTOR (3 downto 0));
```

```
end component;
```

```
component Arithmetic_Unit Port ( a:in std_logic_vector (3 downto 0);
```

```
    b:in std_logic_vector (3 downto 0);
```

```
    s:out std_logic_vector (3 downto 0);
```

```
    add_sub_sel : in STD_LOGIC;
```

```
    C_out : out STD_LOGIC;
```

```
    zero:out std_logic);
```

```
end component;
```

```
component Incrementer Port ( A:in std_logic_vector (2 downto 0);
```

```
    s:out std_logic_vector (2 downto 0));
```

```
end component;
```

```
component Program_Counter Port ( D : in STD_LOGIC_VECTOR (2 downto 0);
```

```
    clk : in STD_LOGIC;
```

```
    res : in STD_LOGIC;
```

```
    q:out std_logic_vector (2 downto 0));
```


end component;

component ROM Port (address : in STD_LOGIC_VECTOR (2 downto 0);

data : out STD_LOGIC_VECTOR (11 downto 0));

end component;

component LUT_16_7 Port (address : in STD_LOGIC_VECTOR (3 downto 0);

data : out STD_LOGIC_VECTOR (6 downto 0));

end component;

component Instruction_Decoder Port (ins : in STD_LOGIC_VECTOR (11 downto 0);

reg_en : out STD_LOGIC_VECTOR (2 downto 0);

load_sel : out STD_LOGIC;

value : out STD_LOGIC_vector (3 downto 0);

mux_1 : out STD_LOGIC_VECTOR (2 downto 0);

mux_2 : out STD_LOGIC_VECTOR (2 downto 0);

aors : out STD_LOGIC;

jmp_flg : out STD_LOGIC;

jmp_add:out std_logic_vector (2 downto 0);

check:in std_logic);

end component;

component mux_2_to_3 Port (r0 : in STD_LOGIC_VECTOR (2 downto 0);

r1 : in STD_LOGIC_VECTOR (2 downto 0);

o : out STD_LOGIC_VECTOR (2 downto 0);

s : in STD_LOGIC);

end component;

component mux_2_to_4 Port (r0 : in STD_LOGIC_VECTOR (3 downto 0);

```

    r1 : in STD_LOGIC_VECTOR (3 downto 0);
    o : out STD_LOGIC_VECTOR (3 downto 0);
    s : in STD_LOGIC);
end component;

component Mux_8_Way_Double Port ( r0 : in STD_LOGIC_VECTOR (3 downto 0);
    r1 : in STD_LOGIC_VECTOR (3 downto 0);
    r2 : in STD_LOGIC_VECTOR (3 downto 0);
    r3 : in STD_LOGIC_VECTOR (3 downto 0);
    r4 : in STD_LOGIC_VECTOR (3 downto 0);
    r5 : in STD_LOGIC_VECTOR (3 downto 0);
    r6 : in STD_LOGIC_VECTOR (3 downto 0);
    r7 : in STD_LOGIC_VECTOR (3 downto 0);
    oa : out STD_LOGIC_VECTOR (3 downto 0);
    ob : out STD_LOGIC_VECTOR (3 downto 0);
    sa : in STD_LOGIC_VECTOR (2 downto 0);
    sb : in STD_LOGIC_VECTOR (2 downto 0));
end component;

signal reg_en:std_logic_vector (2 downto 0);
signal data_mux:std_logic_vector (3 downto 0);
signal r0,r1,r2,r3,r4,r5,r6,r7 :std_logic_vector (3 downto 0);
signal mux4a,mux4b :std_logic_vector (3 downto 0);
signal regmuxa,regmuxb :std_logic_vector (2 downto 0);
signal muxout:std_logic_vector (3 downto 0);
signal addsub:std_logic;
signal imvalue:std_logic_vector (3 downto 0);
signal load_select :std_logic;
signal adder_out:std_logic_vector (2 downto 0);

```

```
signal jmp_add:std_logic_vector (2 downto 0);  
signal jmp_flag:std_logic;  
signal zero_check:std_logic;  
signal s_clk:std_logic;  
signal muxcounterout:std_logic_vector (2 downto 0);  
signal prog_counter:std_logic_vector (2 downto 0);  
signal instruction_bus:std_logic_vector (11 downto 0);
```

```
begin
```

```
slow_clock_1 : Slow_Clock port map(  
    Clk_in=>clk,  
    Clk_out=>s_clk);
```

```
register_bank_1: register_bank port map(  
    clk=>s_clk,  
    en=>reg_en,  
    data=>data_mux,  
    r0=>r0,  
    r1=>r1,  
    r2=>r2,  
    r3=>r3,  
    r4=>r4,  
    r5=>r5,  
    r6=>r6,  
    r7=>r7);
```

```
mux_8_way_double_1: Mux_8_Way_Double port map(  
    r0=>r0,
```

```
r1=>r1,  
r2=>r2,  
r3=>r3,  
r4=>r4,  
r5=>r5,  
r6=>r6,  
r7=>r7,  
oa=>mux4a,  
ob=>mux4b,  
sa=>regmuxa,  
sb=>regmuxb);
```

```
arithmetic_unit_1: Arithmetic_Unit port map(
```

```
  a=>mux4a,  
  b=>mux4b,  
  s=>muxout,  
  add_sub_sel=>addsub,  
  zero=>zero_check,  
  c_out=>overflow);
```

```
mux2to4_1: mux_2_to_4 port map(
```

```
  r0=>muxout,  
  r1=>imvalue,  
  o=>data_mux,  
  s=>load_select);
```

```
mux2to3_1: mux_2_to_3 port map(
```

```
  r0=>adder_out,  
  r1=>jmp_add,
```

```
s=>jmp_flag,  
o=>muxcounterout);
```

```
incrementer_1: Incrementer port map(  
    a=>prog_counter,  
    s=>adder_out);
```

```
instruction_decoder_1: instruction_decoder port map(  
    ins=>instruction_bus,  
    reg_en=>reg_en,  
    load_sel=>load_select,  
    value=>imvalue,  
    mux_1=>regmuxa,  
    mux_2=>regmuxb,  
    aors=>addsub,  
    jmp_flg=>jmp_flag,  
    jmp_add=>jmp_add,  
    check=>zero_check);
```

```
rom_1: rom port map(  
    address=>prog_counter,  
    data=>instruction_bus);
```

```
program_counter_1: Program_Counter port map(  
    d=>muxcounterout,  
    clk=>s_clk,  
    res=>reset,  
    q=>prog_counter);
```

```
led_lut: LUT_16_7 port map(  
    address=>r7,  
    data=>S_7Seg);
```

```
led <= r7;  
zero <= zero_check;
```

```
end Behavioral;
```

Test bench code:

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Uncomment the following library declaration if using  
-- arithmetic functions with Signed or Unsigned values  
--use IEEE.NUMERIC_STD.ALL;
```

```
-- Uncomment the following library declaration if instantiating  
-- any Xilinx leaf cells in this code.  
--library UNISIM;  
--use UNISIM.VComponents.all;
```

```
entity MicroProcessor_Sim is  
    -- Port ( );  
end MicroProcessor_Sim;
```

```
architecture Behavioral of MicroProcessor_Sim is
```

```
    component MicroProcessor Port ( reset : in STD_LOGIC;
```

```

        clk : in STD_LOGIC;

        zero : out STD_LOGIC;

        overflow : out STD_LOGIC;

        led:out std_logic_vector (3 downto 0));
end component;

signal clk:std_logic:='0';
signal reset,zero,overflow:std_logic := '0';
signal led: std_logic_vector (3 downto 0);

begin
MicroProcessor_0 : MicroProcessor port map(
    reset=>reset,
    clk=>clk,
    zero=>zero,
    overflow=>overflow,
    led => led);
process
begin
    clk<=not(clk);
    wait for 1ns;
end process;


process
begin
    reset<='1';
    wait for 5ns;
    reset<='0';
    wait;


```

end process;

end Behavioral;

simulation:

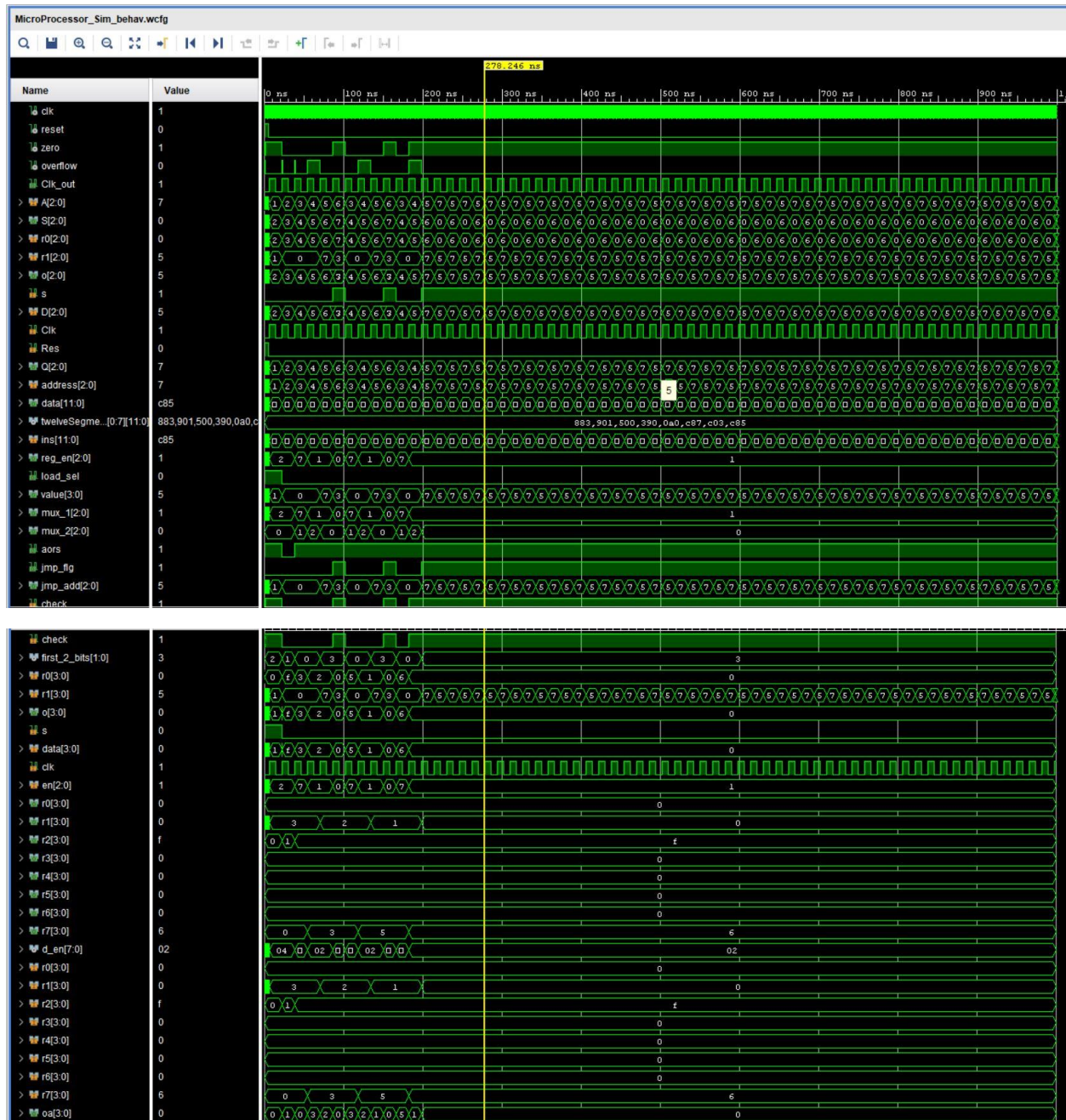

 

➤ Conclusions

- We can build a k-way n-bit MUX by adding n number of k to1 MUXs
- We can larger arithmetic operations by using a larger buses and registers
- We can subtract a number by adding the 2's compliment of that number.
- We can expand the instruction set by expanding the instruction bus.
- We can improve number of instructions by expanding the ROM, program counter
- We cab define a negative flag by checking the MSB of a selected register.